

Design & Construction of Antenna Couplers

Introduction.

When using more than one antenna, a coupler will be needed to take advantage of the increased gain for both antennas. A theoretical value of 3dB increase when doubling the antenna should not be treated as a reachable goal. Several hams use an open feeder system, which will have very good results in coupling.

Unfortunately I have no experience with open feeders, but I can imagine the advantage due to absence of impedance transformers required for coaxial lines.

However, it seems an open feeder system is more sensitive to its climatical environment. For this reason it might need regular maintenance. Imagine your antennas are high in the sky!

So for this only reason I stuck with traditional coaxial interfacing lines between various antennas.

Calculation.

Designing a coupler, some simple calculations and rules are sufficient to perform the job. Using copper plumbing materials will provide you with a sufficient wide choice of tubes to construct an antenna coupler.

RULE: *Impedance transfer must be done in a $\lambda/4$ section.*

The transfer impedance needed in a certain situation can be calculated using following formula:


$$Z_o = \text{SQRT}(Z_a \times Z_t)$$

Where:

Z_o = transfer impedance

Z_a = impedance at side A (usual Antenna side)

Z_t = impedance at side T (usual Tx side)

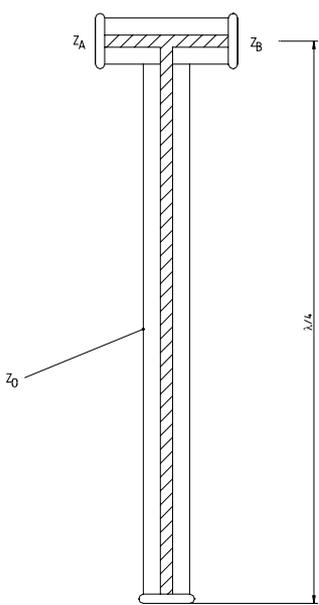	<p>Example 1: Two antennas, each 50 Ohm, must be coupled using besides figure.</p> <p>Solution: The impedance $Z_a = 50 \text{ Ohm} / 2 = 25 \text{ Ohm}$ While $Z_t = 50 \text{ Ohm}$</p> <p>$Z_o = \text{SQRT}(25 \times 50) = 35.4 \text{ Ohm}$</p>
---	---


Example 2:

Two antennas, each 50 Ohm, must be coupled using below construction.

Solution:

The impedance $Z_a = 50 \text{ Ohm}$, while $Z_t = 100 \text{ Ohm}$ in order to match for two antenna sections
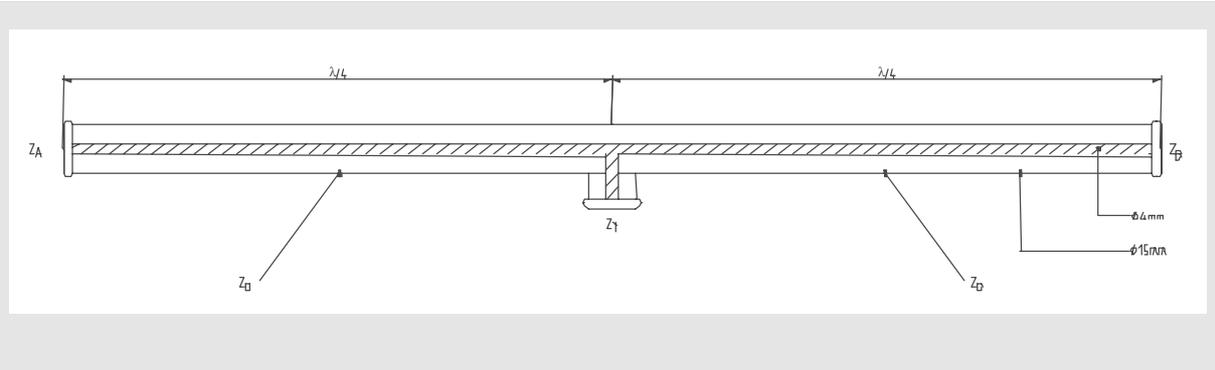
$$Z_o = \text{SQRT}(50 \times 100) = 70.7 \text{ Ohm}$$



Once understanding above type of calculations virtually any combination of antenna's can be coupled.


RULE: Use identical lengths of coaxial cables from the coupler to each antenna.

Construction.


After the calculation is performed several ways of construction can be used to manufacture the coupler. How to create the required transfer impedance Z_o depends on the selected materials.

Below formulas and graphs will help to calculate material dimensions needed.

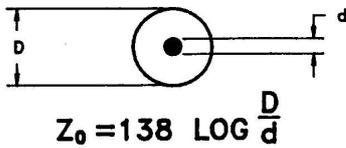
Myself I prefer to use plumbers copper tubes such as 15mm outer diameter. The advantage is that for this type of tubes many additional pieces, T-sections, reduction section etc are available to help in construction.




$$Z_0 = 138 \text{ LOG } \frac{D}{d}$$

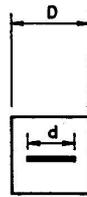
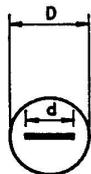
$$Z_0 = 60 \text{ LN } 2.16 \frac{D}{d}$$



$$Z_0 = 60 \text{ LN } 2 \frac{D}{d}$$

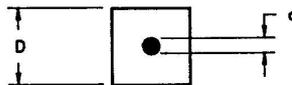

$$Z_0 = 138 \text{ LN } \frac{1.178D}{d}$$

Practical example.

432MHz coupler for two antenna's

$\lambda/4$ wavelength: 17.35cm
Zo : 70.7 Ohm
D/d: 3.3
Outer diameter D: 12 mm copper tube with inside diam: 10mm
Inner diameter d: 3mm

